

Lecture Notes EEE 360

TOPIC 5 Induction Machine


Read Chapter: 8

INDUCTION MOTORS

General

- The induction machine is used as a motor and as a generator. However, it is most frequently used as a motor. It is the Workhorse of industry.
- Majority of the motors used by industry are squirrel cage induction motors.
- Both three-phase and single-phase motors are widely used.
- The induction generators are seldom used. Their typical application is the wind power plant.


Single phase induction motor

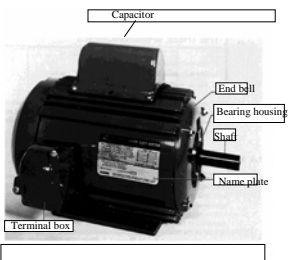

INDUCTION MOTORS


Stator construction

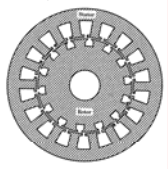- Laminated iron core with slots
- Coils are placed in the slots to form a three or single phase winding



Squirrel-cage rotor construction

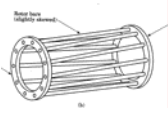- Laminated Iron core with slots
- Metal bars are molded in the slots
- Two rings short circuits the bars
- The bars are slanted to reduce noise




INDUCTION MOTORS

Construction

- The stator has a ring shape laminated iron core with slots.
- A three or single-phase winding is placed in the slots.
- The rotor has a ring-shape laminated iron core, with slots bolted to the shaft.
- **Squirrel Cage Rotor:** Conductor bars are placed in the slots and short circuited at both ends (Most frequently used).

Concept of squirrel cage motor

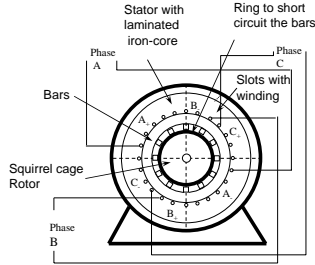

12/10/2007

360 Topic 7 Induction Machine


INDUCTION MOTORS

Construction

Wound-rotor:

- Three-phase windings are placed in the slots.
- The winding is wye or delta connected.
- The ends of each phase is connected to a slip ring.
- Three brushes contact the three slip-rings.
- The rotor winding may be loaded by variable resistance's or supplied by a separate power supply.

Concept of wound-rotor motor

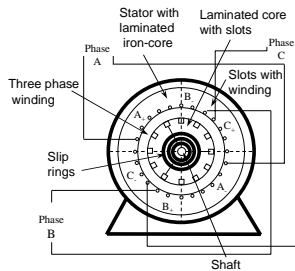

12/10/2007


360 Topic 7 Induction Machine

INDUCTION MOTORS

Stator Construction

- The figure shows a typical stator iron core.
- The laminated ring shaped core is bolted to the motor frame.
- The coils are placed in the slots. The slots are closed by a wedge.
- The coil ends are shaped to fit to the iron core and tied together by strings.
- High voltage motor coils are dried and impregnated.

Stator iron core construction

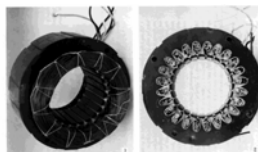

12/10/2007


360 Topic 7 Induction Machine

INDUCTION MOTORS

Stator Construction

- The figure shows typical stator coil construction.
- The coil is wound on a form using insulated (enamel) copper conductors.
- The coil is insulated by insulating tape.
- The insulated coil is placed in the stator slots.
- The two sides of the coil are approximately 180° electrical degree apart.

Stator winding construction

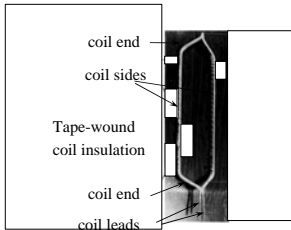

12/10/2007


360 Topic 7 Induction Machine

INDUCTION MOTORS

Squirrel-cage rotor

- The picture shows the rotor of a small and a large motor.
- Both rotors have laminated cores with slots, mounted on a shaft.
- The aluminum bars are slanted on the small rotor. This reduces the noise and improves performance.
- Fins are placed on the ring that shorts the bars. The fins work as a fan and improves cooling.
- The large rotor also has fins and bars. But the bars are not slanted.

Rotor construction

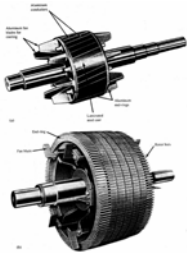

12/10/2007


360 Topic 7 Induction Machine

INDUCTION MOTORS

Wound-rotor

- The picture shows the rotor of a large **wound-rotor motor**
- The ends of each phase is connected to a slip ring.
- Three brushes contact the three slip-rings to three wye connected resistances.

Rotor construction

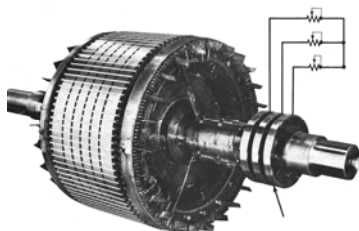

12/10/2007

360 Topic 7 Induction Machine

INDUCTION MOTORS

Three-phase motors. Operation principles.

- The stator is supplied by three-phase voltages that drive three-phase balanced current through the windings.
- The three-phase currents generate a rotating magnetic field.
- The field rotates at synchronous speed. Synchronous speed is determined by the frequency of the supply voltage and the number of poles: $n_s = f / p/2 = 2 f / p$. The unit is rpm.
- The rotating field induces a voltage in the short-circuited rotor conductors.
- The induced voltage generates current in the bars.

12/10/2007

360 Topic 7 Induction Machine

• 10

INDUCTION MOTORS

Three-phase motors. Operation principles

- The interaction between the rotor current and the stator field produces a force that drives the motor: $\text{Force} = B I L \sin \phi$
- The induced voltage magnitude is dependent upon the speed difference between the rotating stator field and the rotor.
- The speed difference is maximum during starting when the motor draws large current. The frequency of the rotor current is 60 Hz when the rotor is stationary.
- As the motor starts to rotate the speed difference is reduced, which results in:
 - reduction on the frequency of the induced voltage in the rotor.
 - reduced magnitude of rotor current and induced voltage.

12/10/2007


360 Topic 7 Induction Machine

• 11

INDUCTION MOTORS

Force generation.

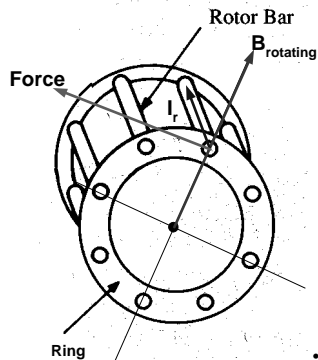- Rotating field induces current in the bar .
- The current and field interaction generates the driving force.
- $\text{Force} = B_{\text{rotating}} L I_r$
- The force drives the motor.
- L is the length of the rotor



12/10/2007

360 Top

• 12

INDUCTION MOTORS

Three-phase motors. Operation principles.

- If the rotor speed is equal to the angular speed of the stator field, the induced voltage, current and torque become zero. Therefore the **motor speed must be less than the synchronous speed.**
- Motor operation requires speed difference between the stator generated rotating field and the actual rotor speed. The speed difference is called **slip (s)** and defined as:

$$s = (n_s - n_r) / n_s \quad \text{where } n_s = 2 f / p$$

- The frequency of the rotor current is: $f_r = s f$
- The slip in normal operation is between 1 and 5 %
- **For demonstration of operation open "Squirrel Cage Rotor" animation program.**

INDUCTION MOTORS

Three phase motors.

Student class room numerical exercise

A three-phase, 20 hp, 208 V, 60 Hz, six pole, wye connected induction motor delivers 15 kW at a slip of 5%.

Calculate:

- Synchronous speed
- Rotor speed
- Frequency of rotor current

Solution

- Synchronous speed: $n_s = 2 f / p = (120) / 6 = 20 \text{ rev/sec} = 1200 \text{ rpm}$
- Rotor speed: $n_r = (1-s) n_s = (1-0.05) (1200) = 1140 \text{ rpm}$
- Frequency of rotor current: $f_r = s f = (0.05) (60) = 3 \text{ Hz}$

INDUCTION MOTORS

Three phase motors. Development of equivalent circuit

- The induction motor consists of a two magnetically connected systems: Stator and rotor.
- This is similar to a transformer that also has two magnetically connected systems: primary and secondary windings.
- The stator is supplied by a balanced three-phase voltage that drives a three-phase current through the winding. This current induces a voltage in the rotor.
- The applied voltage (V_1) across phase A is equal to the sum of the
 - induced voltage (E_1).
 - voltage drop across the stator resistance ($I_1 R_1$).
 - voltage drop across the stator leakage reactance ($I_1 j X_1$).

INDUCTION MOTORS

Three phase motors. Development of equivalent circuit

- The stator voltage equation is:

$$V_1 = E_1 + I_1 (R_1 + j X_1)$$
- The E_1 induced voltage generates a voltage E_2 in the rotor through the magnetic coupling.
 - If the rotor is at stand still, the induced voltage E_2 is proportional to E_1 times the turn ratio. $T = N_{stat} / N_{rot} = N_1 / N_2$. The value is:

$$E_2 = E_1 (N_2 / N_1) = E_1 / T$$
 - If the rotor is rotating, the voltage induced in the rotor is multiplied by the slip s , because the induced voltage is proportional to the speed difference between the stator field and rotor.

$$E_2 = s E_1 / T$$

INDUCTION MOTORS

Three phase motors. Development of equivalent circuit.

- The rotor induced voltage is equal to the sum of the voltage drop across the rotor resistance ($I_2 R_2$), and the leakage inductance ($I_2 X_2$).
- The voltage drop across the secondary leakage inductance L_2 is:

$$I_2 j \omega_2 L_2 = I_2 j (2 \pi f_r) L_2 = I_2 j (2 \pi f) s L_2 = I_2 j s (\omega L_2) = I_2 j s X_2$$

$\swarrow \omega_2$ $\swarrow \omega$ $\swarrow X_2$
- The rotor voltage equation is:

$$E_2 = I_2 (R_2 + j s X_2)$$

INDUCTION MOTORS

Three phase motors. Development of equivalent circuit.

- The equations derived for the induction motors are:

$$V_1 = E_1 + I_1 (R_1 + j X_1)$$

$$E_2 = I_2 (R_2 + j s X_2)$$

$$E_2 = s E_1 / T$$

$$I_2 = I_1 (N_1 / N_2) = I_1 T$$
- Combining the equations we have:

$$E_1 = E_2 T / s = T I_2 (R_2 + j s X_2) / s = I_1 T^2 (R_2 / s + j X_2)$$

$$= I_1 [(R_2 T^2 / s) + j (T^2 X_2)] = I_1 (R_2^* / s + j X_2^*)$$

where: $R_2^* = R_2 T^2$ and $X_2^* = T^2 X_2$ are rotor resistance and reactance referred to the stator.

INDUCTION MOTORS

Three-phase motors. Development of equivalent circuit.

- The derivation results in the following equations:

$$V_1 = E_1 + I_1 (R_1 + j X_1) \quad E_1 = I_1 (R_2^* / s + j X_2^*)$$

- We substitute the second equation into the first one to obtain the following equation for the induction motor:

$$V_1 = I_1 (R_2^* / s + j X_2^*) + I_1 (R_1 + j X_1) = I_1 [(R_1 + R_2^* / s) + j (X_1 + X_2^*)]$$

- The final equation is:

$$V_1 = I_1 [(R_1 + R_2^* / s) + j (X_1 + X_2^*)]$$

INDUCTION MOTORS

Three-phase motors. Development of equivalent circuit.

- The induction motor equation is:


$$V_1 = I_1 [(R_1 + R_2^* / s) + j (X_1 + X_2^*)]$$

- This equation suggests that the induction motor equivalent circuit contains two resistances and reactances connected in series.
- The magnetizing current can be represented by a resistance R_c and a reactance jX_m connected in parallel.
 - The resistance represents the hysteresis and eddy current losses.
 - The reactance represents the magnetizing current that generates the air-gap magnetizing flux.

INDUCTION MOTORS

Three-phase motors. Development of equivalent circuit.

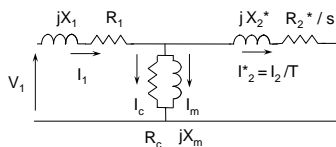- The induction motor equivalent circuit is:




INDUCTION MOTORS

Three-phase motors. Application of equivalent circuit
Student class room exercise.

A three-phase, 20 hp, 220V, 60 Hz, 4 pole, induction motor has the following parameters:

- $R_1 = 0.344 \text{ ohm}$ $X_1 = 0.498 \text{ ohm}$ $X_m = 50 \text{ ohm}$
- $R_2' = 0.224 \text{ ohm}$ $X_2' = 0.344 \text{ ohm}$ $R_c = 500 \text{ ohm}$

Draw the equivalent circuit.

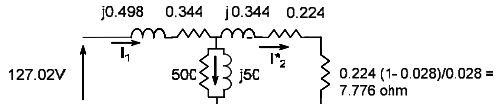

INDUCTION MOTORS

- Draw the equivalent circuit
- Calculate motor impedance vs. slip
- Calculate motor stator and rotor current vs. slip
- Calculate and plot input and output power and efficiency vs. slip
- Calculate motor speed and torque vs. motor speed
- Determine the maximum value of torque, efficiency
- Calculate starting torque

LECTURE 18

INDUCTION MOTORS

Three-phase motors. Determination of parameters from test

- The motor parameters are determined from three tests:
 - No-load test.** Provides the magnetizing reactance and core resistance (R_c and X_m).
 - Blocked-Rotor Test** (Short circuit test). Provides ($R_1 + R_2^*$) and ($X_1 + X_2^*$).
 - Stator DC resistance measurement.** Determines the stator resistance value (R_1).

12/10/2007


360 Topic 7 Induction Machine

INDUCTION MOTORS

Three-phase motors. Determination of parameters from test

- Stator DC resistance measurement**
 - The motor is supplied by DC voltage between two terminals (A and B at the figure).
 - The dc voltage and current are measured.
 - The resistance is:

$$R_1 = \frac{V_{dc}}{2 \cdot I_{dc}}$$

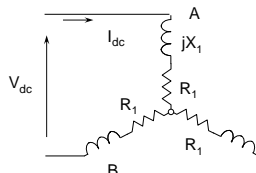

12/10/2007

360 Topic 7 Induction Machine

INDUCTION MOTORS

Three-phase motors. Determination of parameters from test

- No-load test**
 - The motor is supplied by rated line-to-line voltage (V_{nl}) and the no-load current I_{nl} and the no load input power P_{nl} are measured.
 - The no-load input power includes magnetizing and rotational losses.
 - Using the measured values, the admittance and resistance are calculated if the winding leakage impedance is neglected:

$$R_c = \frac{V_{nl}^2}{P_{nl}} \quad \text{and} \quad Y_{nl} = \frac{I_{nl}}{\frac{V_{nl}}{\sqrt{3}}}$$

12/10/2007

360 Topic 7 Induction Machine

INDUCTION MOTORS

Three-phase motors. Determination of parameters from test.

- **No-load test**

- The approximate magnetizing reactance is:

$$X_m = \frac{1}{\sqrt{Y_{nl}^2 - \frac{1}{R_c^2}}}$$

Rotational losses (friction, ventilation etc.) :

- At no-load conditions the slip is very low. Therefore, the rotor copper losses are negligible.
- input power P_{nl} is equal to the core loss and the rotational losses.

INDUCTION MOTORS

Three-phase motors. Determination of parameters from test.

- **Blocked-Rotor Test**


- The motor is supplied by reduced voltage V_{br} (line-to-line) and lower frequency voltage. Approximate frequency value is: $f_{test} = (0.258)(60) = 15$ Hz. Reduced frequency simulates that rotor current frequency is small in normal operation.
- The voltage V_{br} , current I_{br} , the input power P_{br} are measured.
- The rotor is blocked slip is $s = 1$. Magnetizing reactance and resistance are neglected because of reduced supply voltage.

INDUCTION MOTORS

Three-phase motors. Determination of parameters from test.

- **Blocked-Rotor Test**

The approximate equivalent circuit is:

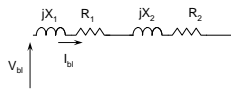

- Blocked rotor resistance is:

$$R_{br} = \frac{P_{br}}{3I_{br}^2}$$

- - Blocked rotor impedance is: $Z_{br} = \frac{V_{br}}{\sqrt{3}I_{br}}$

INDUCTION MOTORS

Three-phase motors. Determination of parameters from test.

- **Blocked-Rotor Test**

- Blocked rotor reactance at the test frequency f_{test} is:

$$X_{br, test} = \sqrt{Z_{br}^2 - R_{br}^2}$$

- Blocked rotor reactance at the rated frequencies:

$$X_{br} = X_{br, test} (f_{rated} / f_{test})$$

- The equivalent circuit parameters are calculated from:

$$R_{br} = R_1 + R_2 \quad \text{and} \quad X_{br} = X_1 + X_2$$

- R_1 is determined by stator resistance measurement.

INDUCTION MOTORS

Determination of motor parameters from test

A three-phase, 30 hp, 208 V, 4 pole, 60 Hz, wye-connected induction motor was tested, obtaining the following data:

- No load at 60 Hz: $V_{nl} = 208 \text{ V}$ $I_{nl} = 22 \text{ A}$ $P_{nl} = 1600 \text{ W}$
- Blocked Rotor at 15 Hz: $V_{br} = 21 \text{ V}$ $I_{br} = 71 \text{ A}$ $P_{br} = 2100 \text{ W}$
- DC test: $V_{dc} = 12 \text{ V}$ $I_{dc} = 75 \text{ A}$

a) Calculate:

- the equivalent circuit parameters
- the rated current and synchronous speed


b) Draw the equivalent circuit with the parameter values.

LECTURE 19

INDUCTION MOTORS

Three-phase motors. Performance Analysis.

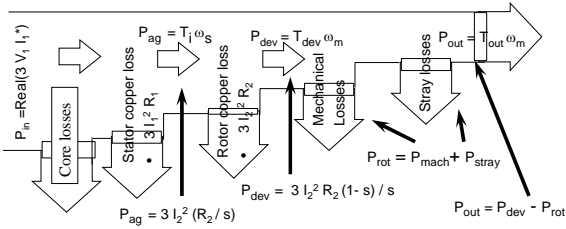- The induction motor performance is evaluated using the equivalent circuit.
- The power flow diagram is shown in the figure:




12/10/2007

360 Topic 7 Induction Machine

INDUCTION MOTORS

Three-phase motors. Torque speed characteristics.

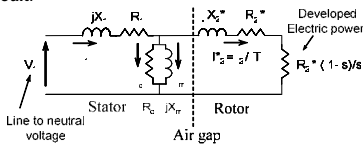- The torque speed relation is calculated from the equivalent circuit.



The electric output or developed power is:

$$P_{Dev} = 3 I_2^2 \frac{1-s}{s} R_2$$

12/10/2007

360 Topic 7 Induction Machine

INDUCTION MOTORS

Three-phase motors. Torque speed characteristics

- The air gap power is:

$$P_{ag} = 3 I_2^2 \frac{R_2}{s}$$

- The synchronous ω is: $\omega_s = 2 \pi n_s = 2 \pi f [2/p]$

- The electromagnetic torque applied to the rotor is:

$$T_e = \frac{P_{ag}}{\omega_s}$$


12/10/2007

360 Topic 7 Induction Machine

INDUCTION MOTORS

Three-phase motors. Torque speed characteristics.

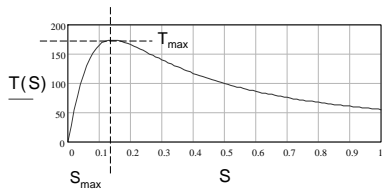- The $T_e(s)$ function can be plotted using the MathCad program.
- The figure shows that the torque has a maximum value.
- The normal operation is between $s = 0$ and s_{max}



12/10/2007

360 Topic 7 Induction Machine

INDUCTION MOTORS

Three-phase motors. Torque speed characteristics

- The output mechanical power is:

$$P_{mech} = 3 I_2^2 \frac{1-s}{s} R_2^* - P_{Rotation}$$

$P_{Rotation}$ are the rotational losses.

- The motor speed ω is: $\omega_m = 2 \pi n_m = 2 \pi n_s (1-s)$

- The output torque is:

$$T_e = \frac{P_{mech}}{\omega_m}$$

12/10/2007

360 Topic 7 Induction Machine

INDUCTION MOTORS

Three-phase motors. Torque speed characteristics.

- The maximum torque is calculated by numerical analysis, or by finding the maximum of the torque function. The steps of the calculation are:
 - Calculation of the torque derivative with respect to slip (s).
 - Setting the derivative to zero and solving the equation for s.

- The result of this calculation is the slip value when the maximum occur.

$$s_{max} = \frac{R_2}{\sqrt{R_1^2 + (X_1 + X_2)^2}}$$

- The maximum torque is calculated by substituting s_{max} into the torque equation.


12/10/2007

360 Topic 7 Induction Machine

INDUCTION MOTORS

Three-phase motors. Starting Torque

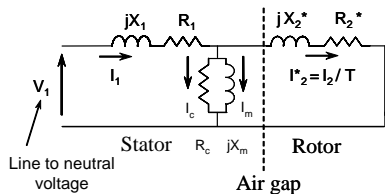- The slip is $s = 1$ at starting.
- The figure show the equivalent circuit at starting.



INDUCTION MOTORS

Three-phase motors. Starting Torque

- The torque is generated by the air-gap power that produces the electromagnetic torque.
- The starting current is the supply voltage divided by the motor impedance. This current is generally 5-6 times the rated current.
- The air gap power is: $P_{ag, start} = 3 R_2 (I_{2start})^2$
- The starting torque is: $T_{start} = P_{ag, start} / \omega_s$

INDUCTION MOTORS

Three-phase motors. Performance Analysis. Example.

- The performance of a motor is demonstrated in an example.
- A three-phase, wye connected, 60 hp, 480 V, 60 Hz, 6 pole, induction motor drives a fan. The motor and fan data are:
- Starting current is 450A, with a power factor of 0.1 lagging.
 - The stator core loss is 1000 W, and the mechanical losses are 650W.
 - At no load, the motor draws 21 A
 - The measured stator resistance between two terminals is : 0.03 ohms
 - The fan torque speed characteristics is:
 - The motor operates with variable slip, verify your equations by $s = 3\%$.
- a) Draw the equivalent circuit.
- b) Calculate: the line current and pf; the electromagnetic, output, and starting torque; and the efficiency. Plot the torque vs. slip curve.

INDUCTION MOTORS

Three-phase motors. Performance Analysis. Example.

The performance of a motor is demonstrated in an example.

A three-phase, wye connected, 60 hp, 480 V, 60 Hz, 6 pole, induction motor:

- Starting current is 450A, with a power factor of 0.1 lagging.
- The stator core loss is 1000 W, and the mechanical losses are 650W.
- At no load, the motor draws 21 A
- The measured stator resistance between two terminals is : 0.03 ohms
- The motor operates with variable slip, verify your equations by $s = 3\%$.

a) Draw the equivalent circuit.

b) Calculate: the line current and pf; the electromagnetic, output, and starting torque; and the efficiency. Plot the torque vs. slip curve.
