

# Lecture Notes EEE 360

## TOPIC 8 DC Machine

Read Chapter: 6.1-6.5, 6.7

10/29/2003

360 Topic 8 DC Machine

1

---

---

---

---

---

---

---

---

# LECTURE 21

10/29/2003

360 Topic 8 DC Machine

2

---

---

---

---

---

---

---


---

# DIRECT CURRENT MACHINES

### DC machine Construction

- The major advantages of DC machines are: easy speed and torque regulation.
- The stator of the DC motor has poles, which are excited by DC current to produce magnetic fields.
- The rotor has a ring-shaped laminated iron-core with slots.
- Coils with several turns are placed in the slots. The distance between the two legs of the coil is about 180 electric degrees.

### Dc motor construction

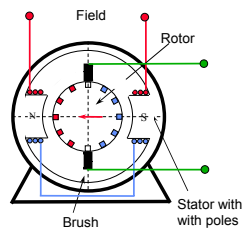

10/29/2003

360 Topic 8 DC Machine

3

---

---

---

---

---

---

---


---

# DIRECT CURRENT MACHINES

## DC machine Construction

- The coils are connected in series.
- The junction points of the coils are connected to a commutator.
- The commutator consists of insulated copper segments mounted in a cylinder.
- Two brushes are pressed to the commutator to permit current flow.
- The brushes are placed in the neutral zone (magnetic field is close to zero) to reduce arcing.

## Concept of the commutator

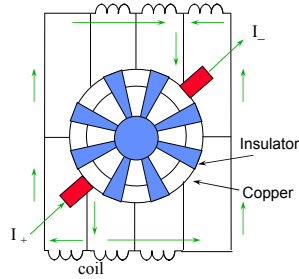

10/29/2003

360 Topic 8 DC Machine

4

---

---

---

---

---

---

---

---

---


---

# DIRECT CURRENT MACHINES

## DC machine Construction

- The picture shows the stator of a large DC machine with several poles.
- Note the interpoles between the main poles. These poles reduce the field in the neutral zone and eliminate arcing of the commutator.
- A compensation winding is placed on the main poles to increase field during high load.
- The iron core is supported by a cast iron frame.

## Dc motor stator construction

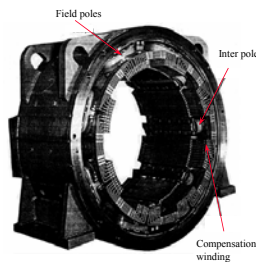

10/29/2003

360 Topic 8 DC Machine

5

---

---

---

---

---

---

---

---

---


---

# DIRECT CURRENT MACHINES

## DC machine Construction

- The adjoining picture shows the rotor of a DC machine.
- The rotor iron core is mounted on the shaft.
- Coils are placed in the slots.
- The end of the coils are bent and tied together to assure mechanical strength.
- Note the commutator mounted on the shaft. It consists of several copper segments, separated by insulation.

## DC motor rotor construction

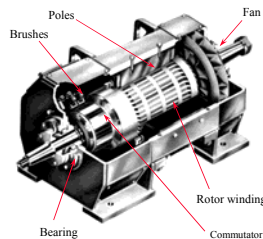

10/29/2003

360 Topic 8 DC Machine

6

---

---

---

---

---

---

---

---


---

---

# DIRECT CURRENT MACHINES
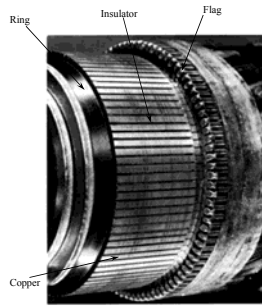
## DC Machine Construction

- The adjoining picture shows the commutator of a large DC machine.
- The segments are made out of copper and mica insulation is placed between the segments.
- The end of each segment has a flag attached. The coil endings are welded to these flags.
- An insulated ring is placed on the coil ends to assure proper mechanical strength.



10/29/2003

360 Topic 8 DC Machine

7

---

---

---

---

---

---

---

---

---


---

# DIRECT CURRENT MACHINES

## Operation principles

- The poles are supplied by DC current producing a DC magnetic field.
- The poles are shaped in such a way the field distribution along the pole is more or less sinusoidal.
- When the rotor coil is rotated, the flux linkage changes during the rotation. It is maximum when the coil is in vertical position and zero when it is in horizontal position.

## DC motor operation concept

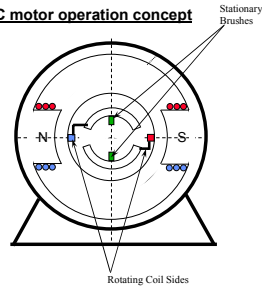

10/29/2003

360 Topic 8 DC Machine

8

---

---

---

---

---

---

---

---


---

---

# DIRECT CURRENT MACHINES
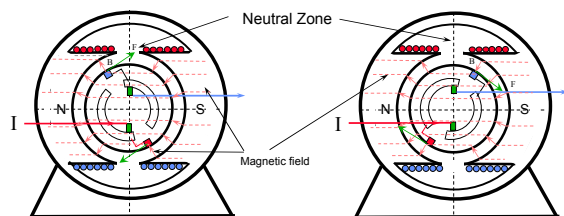
## Concept of commutation

- The current direction changes as the conductor passes through the neutral zone.
- The direction of magnetic field also changes as the conductor passes through the neutral zone.



10/29/2003

360 Topic 8 DC Machine

9

---

---

---

---

---

---

---

---

---

---

# DIRECT CURRENT MACHINES

## Induced voltage and torque calculation.

- The magnetic field is generated by the field current  $I_f$ .
- The flux  $\Phi_f$  is proportional to the field current.  

$$\Phi_f = K_f I_f.$$
- The  $K_f$  factor is calculated from the magnetic circuit using Amperes Law.
- The flux change is proportional to the motor speed  $\omega_m$ .

10/29/2003

360 Topic 8 DC Machine

10

---

---

---

---

---

---

---

---

# DIRECT CURRENT MACHINES

## Induced voltage and torque calculation.

- The induced voltage after rectification is:  

$$E_a = K \Phi_f \omega_m = K K_f I_f \omega_m = K_m I_f \omega_m$$
- The out put power if the losses are neglected is:  

$$P_{dc} = I_a E_a = T_m \omega_m.$$
- The torque is:  

$$T_m = I_a E_a / \omega_m = K \Phi_f I_a = K_m I_f I_a$$

10/29/2003

360 Topic 8 DC Machine

11

---

---

---

---

---

---


---

---

# DIRECT CURRENT MACHINES
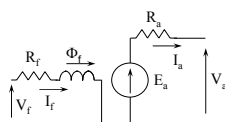
## Equivalent circuit.

- The DC machine can be represented by a voltage source and a resistance connected in series. The armature winding has a resistance,  $R_a$ .
- The field circuit is represented by a winding that generates the magnetic field and a resistance connected in series. The field winding has resistance  $R_f$ .



10/29/2003

360 Topic 8 DC Machine

12

---

---

---

---

---

---

---

---

# DIRECT CURRENT MACHINES

## Equivalent circuit.

The equations are:


$$\Phi_f = K_f I_f$$

$$E_a = K \Phi_f \omega_m = K_m I_f \omega_m$$

$$E_a = V_a + I_a R_a$$

$$V_f = I_f R_f$$

$$T_m = K \Phi_f I_a = K_m I_f I_a$$

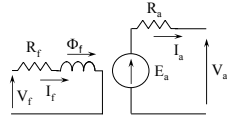

10/29/2003

360 Topic 8 DC Machine

13

---

---

---

---

---

---


---

---

# DIRECT CURRENT MACHINES
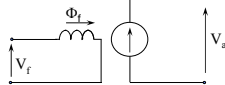
## Type of DC machines.

- **Separately excited machine.**
  - The main winding supplies the load.
  - The field winding is supplied by a separate DC source whose voltage is variable.
  - Good speed control.



10/29/2003

360 Topic 8 DC Machine

14

---

---

---

---

---

---


---

---

# DIRECT CURRENT MACHINES
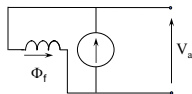
## Type of DC machines.

- **Shunt DC machine.**
  - The armature and field windings are connected in parallel.
  - Constant speed operation.



10/29/2003

360 Topic 8 DC Machine

15

---

---

---

---

---

---


---

---

# DIRECT CURRENT MACHINES
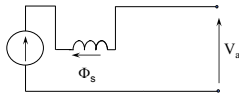
## Major Types of DC machines.

- **Series DC machine.**
  - The armature and field winding are connected in series.
  - High starting torque.



10/29/2003

360 Topic 8 DC Machine

16

---

---

---

---

---

---


---

---

# DIRECT CURRENT MACHINES
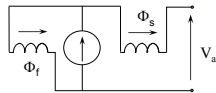
## Major Types of DC machines.

- **Compound DC machine.**
  - The machine has two field windings: One connected in series; the other in parallel.
  - The series winding provides additional, load dependent excitation. Reduced voltage drop at high load.



10/29/2003

360 Topic 8 DC Machine

17

---

---

---

---

---

---

---

---

# DIRECT CURRENT MACHINES


## Numerical Example.

### GENERATOR:

A 20 kW, 250 V, 1300 rpm, separately excited generator has an armature resistance of  $R_a = 0.3$  ohm, and a field coil resistance of  $R_f = 180$  ohms.

- At no load, the terminal voltage is 250 V, the field current is 1.5 A.
- At full load, the terminal voltage is also 250 V.

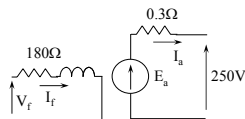- Draw the equivalent circuit.
- At full load, calculate:
  - the generated voltage  $E_a$
  - the developed torque
  - the Field circuit current and voltage



10/29/2003

360 Topic 8 DC Machine

18

---

---

---

---

---

---

---

---

# DIRECT CURRENT MACHINES

## **Numerical Example. GENERATOR:**

- Calculation of the machine constant K from no-load data:
  - Machine speed:  $\omega_m = 2 p n / 60 = 2 p 1300 / 60 = 136.13 \text{ 1/sec}$
  - Machine constant:  $E_{a, nl} = K \Phi_f \omega_m = K_m I_f \omega_m$   
 $K_m = E_{a, nl} / I_f \omega_m = 250 / (1.5)(136.13) = 1.224$
- Load current:  $I_a = 20000 / 250 = 80 \text{ A}$

---

---

---

---

---

---

---

---

# DIRECT CURRENT MACHINES

## **Numerical Example. GENERATOR.**

- Generated voltage:  
 $E_a = V_t + I_a R_a = 250 + (80)(0.3) = 274 \text{ V}$
- Torque:  
 $T_e = E_a I_a / \omega_m = (274)(80) / 136.131 = 161.0 \text{ Newton m}$
- Excitation/ field current and voltage at full load:  
 $I_f = E_a / (K_m \omega_m) = 274 / (1.224)(136.131) = 1.64 \text{ A}$   
 $V_f = R_f I_f = (1.64)(180) = 296 \text{ V}$

---

---

---

---

---

---

---

---

# LECTURE 22

---

---

---

---

---

---

---

---

# DIRECT CURRENT MACHINES

**Motor speed characteristics**  
**Numerical Example**

- Motor equations  
 $E_a = K_m I_f \omega_m$   
 $E_a = V_a - I_a R_a - V_{brush}$   
 $V_f = I_f R_f$   
 $T_m = K_m I_f I_a$

The first two equations yield:

$$\omega_m = \frac{V - V_{brush} - \frac{R_a \cdot I_a}{K_m I_f}}{K_m I_f}$$

---

---

---

---

---

---

---

---

# DIRECT CURRENT MACHINES

**Motor speed characteristics.**


The substitution of  $I_a$  from the fourth equation results in :

$$\omega_m = \frac{V - V_{brush}}{K_m I_f} - \frac{R_a}{(K_m I_f)^2} \cdot T_m$$

$$\omega_m = \frac{300}{0.9352} - \frac{0.2}{(0.9352)^2} \cdot T_m$$

$$\omega_m = 140.25 - 0.0571 \cdot T_m$$

$$T_m = 2456.21 + 17.51 \omega_m$$

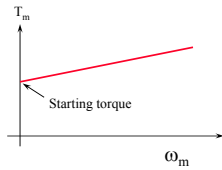


---

---

---

---

---

---

---

---

# DIRECT CURRENT MACHINES


**Motor starting**  
**Numerical Example**

- This current is too high. It must be limited to 2-3 times the rated current by a resistance connected in series with the armature.

$$2 I_a = (2)(62.3) = (300-4)/(0.2+R)$$

From this equation  $R = 2.17 \text{ ohm}$

Equivalent circuit for starting

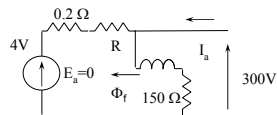


---

---

---

---

---

---

---


---

# DIRECT CURRENT MACHINES

## Motor starting
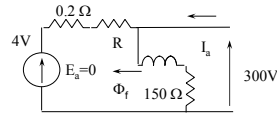
### Numerical Example

- The torque equation is :  $T_m = K_m I_f I_a$
- The starting torque is  $T_m = (0.935)(2)(124.8) = 233.4$  Newton m
- The  $K_m$  is calculated from the no-load data.  
 $K_m = 0.935$  Vsec / A
- The field current is :  $300 / 150 = 2$  A
- The load current is :  $(300-4) / (0.2+2.17) = 124.8$  A



10/29/2003

360 Topic 8 DC Machine

25

---

---

---

---

---

---

---

---


# DIRECT CURRENT MACHINES

## Numerical Example
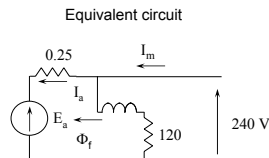
### MOTOR.

A 15 kW, 240 V, shunt motor has an armature resistance of  $R_a = 0.25$  ohm, and a field coil resistance of  $R_f = 120$  ohms. At rated terminal voltage the motor current is 8 A and runs at 1000 rpm.

- Draw the equivalent circuit.
- Calculate the motor constant
- Calculate the speed and torque characteristics



10/29/2003

360 Topic 8 DC Machine

26

---

---

---

---

---

---

---

---

# DIRECT CURRENT MACHINES

## Numerical Example.

### MOTOR.

- Calculation of field current:  
 $I_f = 240 / 120 = 2$  A
- The armature current at no load is:  
 $I_a = 8 - 2 = 6$  A
- Generated voltage at no load is:  
 $E_a = V_t - I_a R_a = 240 - (6)(0.25) = 238.5$  V
- No load speed:  
 $\omega_{m,nl} = 2 \pi n / 60 = 2 \pi (1000) / 60 = 104.72 / \text{sec}$

10/29/2003

360 Topic 8 DC Machine

27

---

---

---

---

---

---

---

---

# DIRECT CURRENT MACHINES

## Numerical Example

### MOTOR.

- Machine constant:

$$E_a = K \Phi_f \omega_{m,nl} = K_m I_f \omega_{m,nl}$$

$$K_m = E_a / I_f \omega_{m,nl} = 238.5 / (2) (104.72) = 1.139$$

- Load current:

$$I_m = 15000 / 240 = 62.5 \text{ A}$$

- The armature current is:

$$I_a = 62.5 - 2 = 60.5 \text{ A}$$

10/29/2003

360 Topic 8 DC Machine

28

---

---

---

---

---

---

---

---

# DIRECT CURRENT MACHINES

## Numerical Example.

### MOTOR.

- Generated voltage at full load is:

$$E_a = V_t - I_a R_a = 240 - (60.5)(0.25) = 224.9 \text{ V}$$

- Motor speed at full load:

$$E_a = K \Phi_f \omega_m = K_m I_f \omega_m$$

$$\omega_m = E_a / K_m I_f = 224.8 / (1.139)(2) = 98.8 \text{ rad./sec}$$

$$n_m = 60 \omega_m / 2 \pi = 942.7 \text{ rpm.}$$

- Torque:

$$T_e = E_a I_a / \omega_m = (224.8)(60.5) / 98.8 = 137.65 \text{ Newton m}$$

10/29/2003

360 Topic 8 DC Machine

29

---

---

---

---

---

---

---

---

# DIRECT CURRENT MACHINES

## Motor starting.

### Numerical Example


- a) Calculate the starting current of the previous example.

- The induced voltage is zero because the speed is zero.

- The starting current is :

$$I_{\text{start}} = (300 - 4) / 0.2 = 1480 \text{ A.}$$

Equivalent circuit for starting

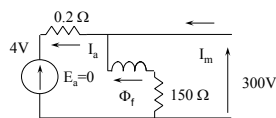

10/29/2003

360 Topic 8 DC Machine

30

---

---

---

---

---

---

---

---


# DIRECT CURRENT MACHINES

## Student Class Room Exercise

### Numerical Example

A 25 Hp, 300V, shunt motor has an armature resistance of  $R_a = 0.20$  ohm, and a field coil resistance of  $R_f = 150$  ohms. The brush voltage drop is 4 V. At no load and rated voltage, the motor current is 13 A and the speed is 1500 rpm.

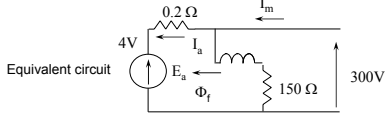- a) Draw the equivalent circuit.
- b) Calculate the speed and torque at full load.



10/29/2003

360 Topic 8 DC Machine

31

---

---

---

---

---

---

---

---

# DIRECT CURRENT MACHINES

## Questions to ponder

- For each of the basic types of DC motors (shunt, series, compound) which is used for railways?
- What type of motor is recommended for electric cars?
- How is the speed of electric cars controlled?
- What type of motor would you select for conveyor belt, punch press and fan?
- What are the components of a DC drive system?

10/29/2003

360 Topic 8 DC Machine

32

---

---

---

---

---

---

---

---

# TEST 4

## Induction Machine

10/29/2003

360 Topic 8 DC Machine

33

---

---

---

---

---

---

---

---

# LECTURE 23

10/29/2003

360 Topic 8 DC Machine

34

---

---

---

---

---

---

---

---

## DC shunt motor

A dc shunt motor is supplied through a feeder with a battery. The motor drives a pump.

Motor data are  $\text{rpm} := \text{min}^{-1}$

$P_{\text{rated}} := 1\text{hp}$     $V_{\text{rated}} := 24\text{V}$     $R_A := 0.1\Omega$     $R_f := 10\Omega$

Motor is tested and the test results are:

$V_{\text{test}} := V_{\text{rated}}$     $I_{\text{test}} := 90\text{A}$     $n_{\text{test}} := 850\text{rpm}$

Battery and feeder data are:

$V_{\text{batt}} := 25\text{V}$     $R_{\text{batt}} := 0.1\Omega$     $R_{\text{feeder}} := 0.2\Omega$

The pump torque vs speed characteristics  $n := 600\text{rpm}$

$a := 1\text{N}\cdot\text{m}$     $b := 0.002\text{N}\cdot\text{m}\cdot\text{sec}^2$     $T_{\text{pump}}(n) := a + b\cdot n^2$     $T_{\text{pump}}(n) = 1.2\text{N}\cdot\text{m}$

$P_{\text{pump}}(n) := T_{\text{pump}}(n) \cdot 2\pi \cdot n$     $P_{\text{pump}}(n) = 0.101\text{hp}$     $T_{\text{pump}}(0\text{rpm}) = 1\text{J}$

- 1) Draw the equivalent circuit and calculate motor parameters
- 2) Calculate the currents and voltages as a function of the speed
- 3) Plot the motor and pump torque vs. speed characteristics
- 4) Determine to operation point, speed and torque

10/29/2003

360 Topic 8 DC Machine

35

---

---

---

---

---

---

---

---

## DC Series motor operation analysis

A 40 kW, 240 V, series motor has an armature resistance of  $R_A = 0.25\text{ohm}$ , and a field coil resistance of  $R_f = 0.3\text{ohms}$ .

The motor current, speed and voltage are measured to determine the motor constant. The measured values are: At rated terminal voltage the motor current is 8 A and runs at 500 rpm. Derive the motor operation characteristics, which are efficiency vs. speed, torque vs. speed.

Data of the shunt motor are:  $\text{rpm} := \frac{1}{\text{min}}$

Rated values

$P_m := 26\text{kW}$     $V_{dc} := 240\text{V}$     $R_A := 0.25\Omega$     $R_f := 0.3\Omega$

Measured values for motor constant calculation

$I_{ms} := 8\text{A}$     $n_{ms} := 500\text{rpm}$     $V_{ms} := V_{dc}$

Draw the motor equivalent circuit in no-load condition to determine the motor constant

10/29/2003

360 Topic 8 DC Machine

36

---

---

---

---

---

---

---

---