



Q1

(a) The load on a 460-V, 60Hz, Y-connected balanced three-phase source consists of three equal Y-connected impedances of $100+j100$ Ohms connected in parallel with three Delta connected impedances of $300-j300$ Ohms. Compute:

- (1) The line current of the total load.
- (2) The total load power
- (3) The power factor of the total load

(b) Two wattmeters are used measure power in a balanced wye-wye system. The line voltage is 208-V. Wattmeter A reads 1600 W and wattmeter B reads 840 W. Compute the impedance per phase.

a)

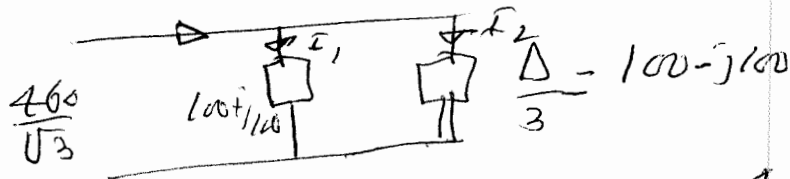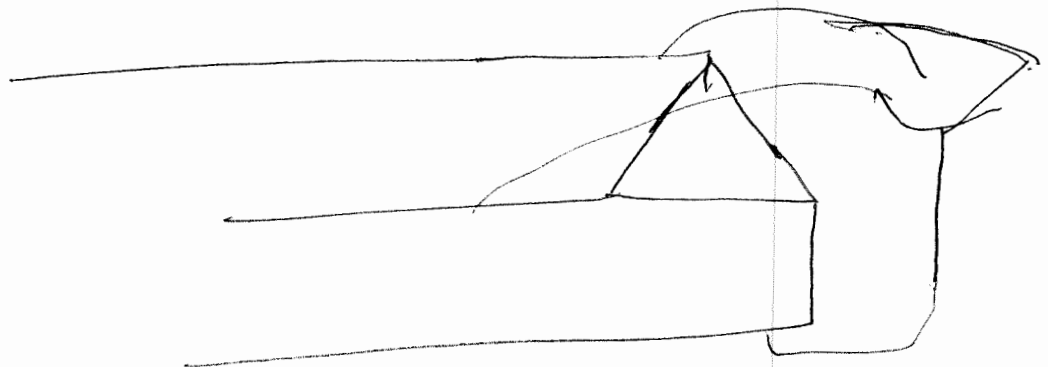

$$I_1 = \frac{460}{\sqrt{3}(100+j100)} \quad I_2 = \frac{460}{\sqrt{3}(100-j100)}$$

$$(i) I_T = I_1 + I_2 = \frac{265.6}{100} = 2.656 A$$

$$(ii) P_T = \sqrt{3}(460)(2.656) = 2116 W$$

$$(iii) PF = 1.0$$

b)

$$P_T = P_A + P_B = 1600 + 840 = 2440 W$$

$$\theta = \tan^{-1} \left[\frac{P_A - P_B}{P_A + P_B} \right] \sqrt{3} = \tan^{-1} \left[\frac{760}{2440} \right] \sqrt{3} = 28.32^\circ$$


$$PF = 0.8803 \quad P_T = \sqrt{3} V_L I_L PF; \quad I_L = 7.694; \quad Z = \frac{V_P}{I_P} = \frac{208}{\sqrt{3}(7.694)}$$

$$= 15.61 \angle 28.35^\circ$$

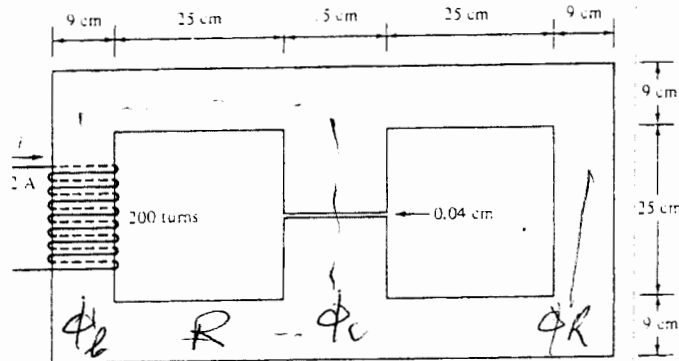Q2 (a) A magnetic core is shown in the figure below. Its depth is 5 cm and there are 200 turns on the leftmost leg. The relative permeability of the core is 1200.

Calculate:

- The flux in each of the three legs.
- The flux density in each of the three legs..



(b) The eddy current loss of a given solid core is 80 W at 50Hz. What would be the loss at 60 Hz if the maximum flux density remained the same at the two frequencies.

a)

$R_1 = \text{reluctance of left.}$
 $R_2 = \text{reluctance of Right.}$
 $R_3 = \text{center; } R_4 = \text{air gap}$

$$R_T = R_1 + \frac{R_2(R_3 + R_4)}{R_2 + R_3 + R_4}; \quad R_1 = \frac{l_1}{\mu_0 \mu_r A} = \frac{1.08}{1200(4\pi \times 10^{-7})(0.09 \times 0.05)} = 159 \text{ kAT}$$

$$R_2 = 159 \text{ kAT/Wb}$$

$$R_3 = \frac{0.34}{1200(4\pi \times 10^{-7})0.15(0.05)} = 30.0 \text{ kA-T/Wb.}$$

$$R_4 = \frac{0.004}{4\pi \times 10^{-7}(0.15)(0.05 \times 1.0)} = 42.4 \text{ kA-T/Wb}$$

$$R_T = 209 \text{ kAT/Wb}; \quad \Phi_T = \frac{NI}{R} = 0.0019 \text{ Wb}$$

CDR; $\Phi_C = 0.0013$; $\Phi_L = 0.0019$; $\Phi_R = 0.0006$

$$B_L = \frac{\Phi_L}{A} = 0.42 \text{ T}; \quad B_C = 0.17; \quad B_R = 0.13$$

$E_{\text{eddy}} = k_f f^2 B_{\text{max}}^2$
 $80 = k_f (50)^2 B_{\text{max}}^2$
 $E_2 = k_f (60)^2 B_{\text{max}}^2$
 $\therefore E_2(60) = 80 \left(\frac{60}{50}\right)^2 = 115.2 \text{ W}$

(b)

Q3

(a) Choose the correct answer

A transformer having 1000 primary turns is connected to a 250-V AC supply. For a secondary voltage of 400 V, the number of secondary turns should be:

a. 250

B. 1600

c. 400

d. 1250

50

(b) The secondary voltage of a transformer is $V_2(t) = 282.8 \sin 377t$. The turns ratio is 50:200. If the secondary current is $I_2(t) = 7.07 \sin(377t - 36.8)$.

(i) What is the primary voltage of the transformer? 5

(ii) What is the primary current of the transformer? 5

(iii) What is the power rating of the transformer? 5

$$V_2 = \frac{282.8}{\sqrt{2}} = 200V$$

$$I_2 = \frac{7.07}{\sqrt{2}} = 5$$

$$(i) \frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{50}{200} \quad \therefore \underline{V_1 = 50V}$$

$i_1(t) = 7.07 \sin 377t$

$$(ii) \frac{I_1}{I_2} = \frac{N_2}{N_1}; \quad I_1 = 20A; \quad i_1(t) = 28.28 \sin(377t - 36.8)$$

$$(iii) V_1 I_1 = 50 \times 20 = 1000VA = \underline{\underline{800Watt}}$$