

EE 360 ELECTRIC Energy

LECTURE 01

Introduction to 3 Phase circuits

The material covered in this lecture will be as follows:

- ⇒ To understand how to generate three phase voltage sources.
To understand how to generate three phase voltage sources.
- ⇒ To know how to connect three phase balanced circuits in Wye and delta configurations.
To know how to connect three phase balanced circuits in Wye and delta configurations
- ⇒ To analyze three phase circuits connected as Wye-Wye
To analyze three phase circuits connected as Wye-Wye
- ⇒ To analyze three phase circuits connected as Wye-Delta
To analyze three phase circuits connected as Wye-Delta

At the end of this lecture you should be able to:

- ⇒ Understand the relationship between the three phase voltages in a balanced circuit
Understand the relationship between the three phase voltages in a balanced circuit
- ⇒ Find the line and phase voltages & currents in balanced Wye-Wye circuits
Find the line and phase voltages & currents in balanced Wye-Wye circuits
- ⇒ Find the line and phase voltages & currents in balanced Wye- Delta circuits
Find the line and phase voltages & currents in balanced Wye- Delta circuits

Generation of Three Phase Voltages

Electricity is generated, transmitted, distributed and utilized in what is known as three phase system.

Electricity is generated, transmitted, distributed and utilized in what is known as three phase system

It is therefore essential to understand the concepts of three phase system. We will start from the single phase concept.

It is therefore essential to understand the concepts of three phase system. We will start from the single phase concept.

If a single coil is rotated at a constant speed in a magnetic field, an alternating voltage is produced.

If a single coil is rotated at a constant speed in a magnetic field, an alternating voltage is produced.

The voltage is function of time, speed of rotation, and a maximum value.

The voltage is function of time, speed of rotation, and a maximum value.

The voltage has the following mathematical form

The voltage has the following mathematical form

$$v(t) = V_m \sin(\omega t)$$

Where

V_m = the maximum voltage or amplitude in volts.

V_m = the maximum voltage or amplitude in volts.

ω = frequency in radians per second.

ω = frequency in radians per second.

$$= 2 * \pi * f$$

f = frequency in number of cycles per second or Hertz per second.

f = frequency in number of cycles per second or Hertz per second.

The frequency of the supply in Saudi Arabia is 60 Hertz per seconds.

The frequency of the supply in Saudi Arabia is 60 Hertz per seconds.

In most countries it is 50 Hertz per second.

In most countries it is 50 Hertz per second.

Fig-1 shows a graphical display of the voltage generated as function of time.

Fig-1 shows a graphical display of the voltage generated as function of time

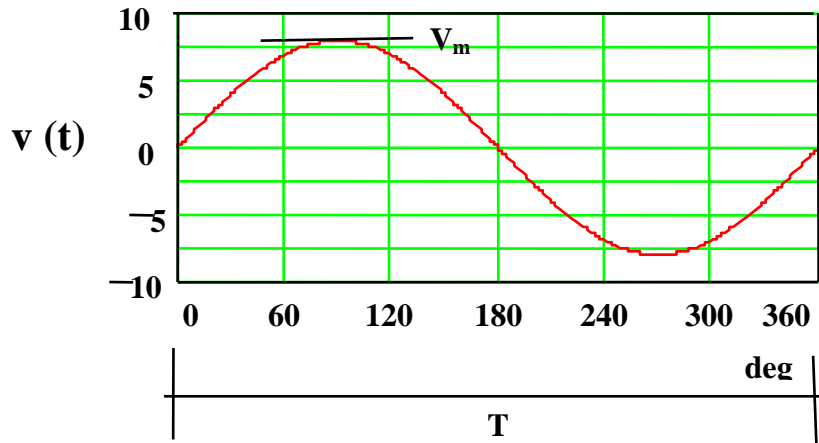


Figure 1

If three coils (a, b &c) , each occupying 120 degrees in space, are rotated at the same speed within the same magnetic , they will produce identical voltages except that they are shifted from each other by 120 degrees.

If three coils (a, b &c) , each occupying 120 degrees in space, are rotated at the same speed within the same magnetic , they will produce identical voltages except that they are shifted from each other by 120 degrees.

Mathematically these are represented as follows:

Mathematically these are represented as follows:

$$v_a(t) = V_m \sin(\omega t) \quad (1)$$

$$v_b(t) = V_m \sin(\omega t - 120) \quad (2)$$

$$v_c(t) = V_m \sin(\omega t - 240) \quad (3)$$

These are referred to as balanced three phase voltages.

These are referred to as balanced three phase voltages.

Fig-2 shows a graphical display of the voltage generated as function of time.

Fig-2 shows a graphical display of the voltage generated as function of time.

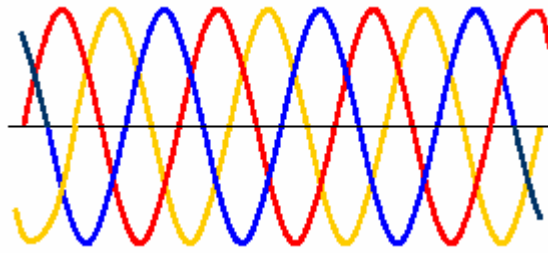


Figure 2

For the purpose of circuit analysis, frequency domain and phasor representation are used.

For the purpose of circuit analysis, frequency domain and phasor representation are used.

Each sinusoidal signal is represented by its equivalent rms and its angular shift from a reference signal.

Each sinusoidal signal is represented by its equivalent rms and its angular shift from a reference signal.

The rms of the sinusoidal signal is given as follow

The rms of the sinusoidal signal is given as follow

$$V = V_m / \sqrt{2} \quad (4)$$

Using phase a as a reference, the three phase system can be described as follows:

Using phase a as a reference, the three phase system can be described as follows:

$$V_a = V \angle 0^\circ$$

$$V_b = V \angle -120^\circ$$

$$V_c = V \angle -240^\circ$$

Fig-3 shows a the phasor representation of 3 phase voltages referred to phase a.

Fig-3 shows a the phasor representation of 3 phase voltages referred to phase a

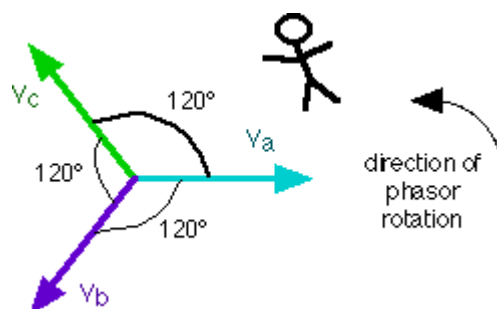


Figure 3

Wye and Delta Connections

Wye and Delta Connections

Each coils has two ends: a start and an end.

Each coils has two ends: a start and an end.

For a 3 phase system this means there is a need for six conductors

For a 3 phase system this means there is a need for six conductors

In order to reduce the conductor losses, it is essential to reduce the number of conductors.

This is achieved by connecting the coils, or phases, in either of two forms.

This is achieved by connecting the coils, or phases, in either of two forms.

These are called Wye and Delta connections.

These are called Wye and Delta connections.

However, before we describe the Wye and delta connections, it is important to make the following definitions

However, before we describe the Wye and delta connections, it is important to make the following definitions

Phase

describes one element or device in a load, line, or source. It is simply a "branch" of the circuit..

Phase

describes one element or device in a load, line, or source. It is simply a "branch" of the circuit..

Line

refers to the "transmission line" or wires that connect the source (supply) to the load.

Line

refers to the "transmission line" or wires that connect the source (supply) to the load.

Neutral

the 4th wire in the 3-phase system. It's where the phases of a Wye connection come together.

Neutral

the 4th wire in the 3-phase system. It's where the phases of a Wye connection come together

Phase Voltages & Phase Currents

The voltages and currents across and through a single branch (phase) of the circuit.

Phase Voltages & Phase Currents

The voltages and currents across and through a single branch (phase) of the circuit.

Line Currents

The currents flowing in each of the lines (I_a , I_b , and I_c).

Line Currents

The currents flowing in each of the lines (I_a , I_b , and I_c).

Line Voltages

The voltages between any two of the lines (V_{ab} , V_{bc} , and V_{ca}). These may also be referred to as the line-to-line voltages.

Line Voltages

The voltages between any two of the lines (V_{ab} , V_{bc} , and V_{ca}). These may also be referred to as the line-to-line voltages.

Line to Neutral Voltages

The voltages between any lines and the neutral point (V_a , V_b , and V_c). .

Line to Neutral Voltages

The voltages between any lines and the neutral point (V_a , V_b , and V_c). .


a. Wye (Y or Star) Connection
Wye (Y or Star) Connection

The ends of the three phases are connected together to form the neutral while the other ends (or terminals form the line connections.

The ends of the three phases are connected together to form the neutral while the other ends (or terminals form the line connections

Figure 4 shows the Wye or star connection of a 3 phase system

Figure 4 shows the Wye or star connection of a 3 phase system

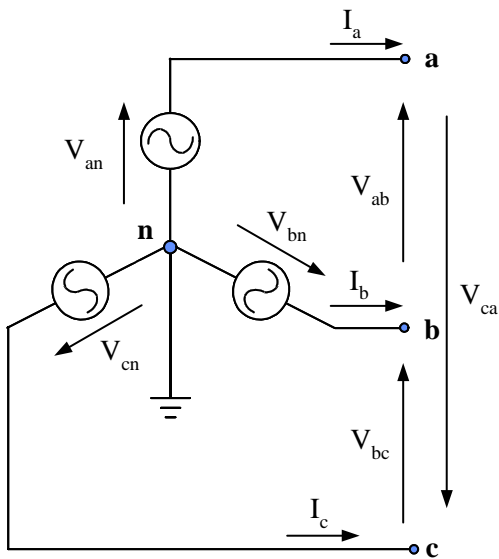

Let us determine the relationships between the line and phase voltages.

Let us determine the relationships between the line and phase voltages.

$$V_{ab} = V_a - V_b \quad (8)$$

$$V_{ab} = V\angle 0 - V\angle -120$$

$$V_{ab} = V(1 - 1\angle -120)$$

$$= V(1 - \cos(120) - j \sin(120))$$

$$= V(1 - (-1/2) + j(\sqrt{3}/2)) = V(3/2 + j(\sqrt{3}/2))$$

Converting to polar form and re-arranging the terms.

Converting to polar form and re-arranging the terms

$$V_{ab} = V_a * \sqrt{3}\angle 30^\circ \quad (9)$$

This result is states as follows

This result is states as follows

The line to line voltage is related is related to the phase voltage by a factor of $\sqrt{3}$ and it leads it by an angle of 30 degrees.

The line to line voltage is related is related to the phase voltage by a factor of $\sqrt{3}$ and it leads it by an angle of 30 degrees.

Also the currents in lines are the same as those flowing through the phase.

Also the currents in lines are the same as those flowing through the phase.

This is stated as line current is always equal to the phase current.

This is stated as line current is always equal to the phase current.

$$I_l = I_p \quad (10)$$

Example 1

Let us assume that the phase voltage is 120-V. Find the line voltage?

Let us assume that the phase voltage is 120-V. Find the line voltage?

$$V_a = 120\angle 0^\circ$$

$$V_b = 120\angle -120^\circ$$

$$V_{ab} = 120\angle 0 - 120\angle -120$$

$$V_{ab} = 120(1 - 1\angle -120)$$

$$V_{ab} = 120 * \sqrt{3}\angle 30^\circ$$

$$V_{ab} = 207.85\angle 30^\circ$$

$$V_{bc} = 207.85\angle -90^\circ$$

$$V_{ca} = 207.85\angle -210^\circ$$

We say that the voltage between the lines is 208 volts (rounding up), and thus the power system voltage is designated as 120/208-V.

We say that the voltage between the lines is 208 volts (rounding up), and thus the power system voltage is designated as 120/208-V

Loads in a facility such as a building, a factory and others may also be arranged in 3 phase configurations.

Loads in a facility such as a building, a factory and others may also be arranged in 3 phase configurations.

They can be connected in a Wye or star configurations.

They can be connected in a Wye or star configurations.

Fig 5 shows a Wye connected source supplying a Wye-connected load. This system is referred to a 3-wire System. The neutral points are not connected together. This system is not widely used.

Fig 5 shows a Wye connected source supplying a Wye-connected load. This system is referred to a 3-wire System. The neutral points are not connected together. This system is not widely used.

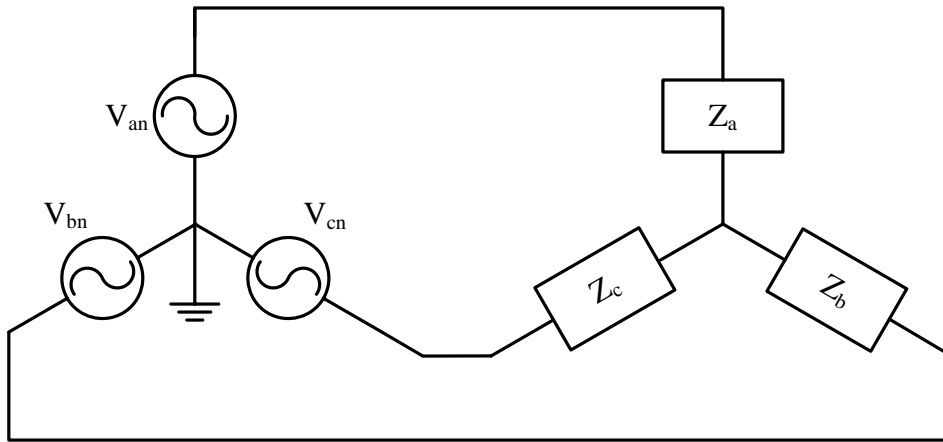


Fig 5

Fig 6 shows a Wye connected source supplying a Wye-connected load with the two neutrals connected. This system is referred to a 4-wire.

Fig 6 shows a Wye connected source supplying a Wye-connected load with the two neutrals connected. This system is referred to a 4-wire.

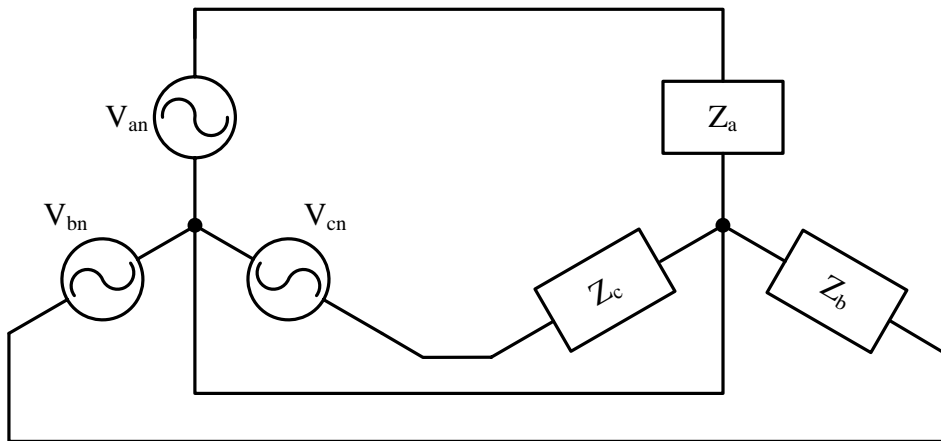


Figure 6.

In a 4-wire system, the following relationship can be written:

$$I_a = \frac{V_{an}}{Z_a} \quad I_b = \frac{V_{bn}}{Z_b} \quad I_c = \frac{V_{cn}}{Z_c} \quad (11)$$

Having a balanced circuit allows for simplified analysis of the 3-phase circuit.

Having a balanced circuit allows for simplified analysis of the 3-phase circuit.

Following are the requirements that must be satisfied in order for a 3-phase system or circuit to be balanced.

Following are the requirements that must be satisfied in order for a 3-phase system or circuit to be balanced

1. All 3 sources are represented by a set of balanced 3-phase variables

All 3 sources are represented by a set of balanced 3-phase variables

2. All loads are 3-phase with equal impedances

All loads are 3-phase with equal impedances

3. Line impedances are equal in all 3 phases

Line impedances are equal in all 3 phases

If the circuit is balanced, we can solve for the voltages, currents, and powers, etc. in one phase using circuit analysis.

If the circuit is balanced, we can solve for the voltages, currents, and powers, etc. in one phase using circuit analysis.

This is called equivalent single phase.

This is called equivalent single phase.

If the circuit is not balanced, all three phases should be analyzed in details. This is not addressed in this chapter.

If the circuit is not balanced, all three phases should be analyzed in details. This is not addressed in this chapter.

Example 2

A 4-wire Y-connected 3-phase 120/208-V source is connected to Y-connected balanced load. The impedance per phase is $12\angle 30^\circ \Omega$. Find

- (i) the phase and line voltages at the load
- (ii) the phase and line currents through the load.

Solution

Using Phase a as a reference

Using Phase a as a reference

- (i) The phase voltage at the load are given as follows:

The phase voltage at the load are given as follows:

$$V_{an} = 120 \angle 0^\circ$$

$$V_{bn} = 120 \angle -120^\circ$$

$$V_{cn} = 120 \angle -240^\circ$$

The line-line voltages at the load are given by:

The line-line voltages at the load are given by:

$$V_{ab} = 207.85 \angle 30^\circ$$

$$V_{bc} = 207.85 \angle -90^\circ$$

$$V_{ca} = 207.85 \angle -210^\circ$$

(ii) In Y-connected load, the phase and line currents are equal.

In Y-connected load, the phase and line currents are equal

$$I_a = \frac{V_{an}}{Z_a}$$

$$I_a = 120 \angle 0^\circ / 12 \angle 30^\circ$$

$$I_a = 10 \angle -30^\circ \text{ A.}$$

Similarly the phase currents of phases b & c are given as follows:

Similarly the phase currents of phases b & c are given as follows:

$$I_b = 10 \angle -150^\circ \text{ A}$$

$$I_c = 10 \angle -270^\circ \text{ A}$$

b. Delta (or Δ) Connection

Delta (or Δ) Connection

The end of one phase is connected to the start of another phase to form a closed loop referred to as delta connection.

The end of one phase is connected to the start of another phase to form a closed loop referred to as delta connection.

Figure 7 shows a typical Δ connection of sources.

Figure 7 shows a typical Δ connection of sources.

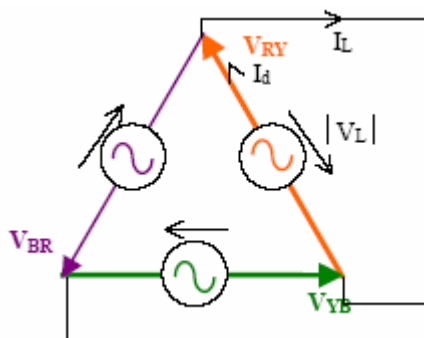


Fig 7

As shown in Figure 7, The line voltage V_{ab} is equal to phase voltage V_a .

As shown in Figure 7, The line voltage V_{ab} is equal to phase voltage V_a .

However, for the purposes of analysis, Delta connected source are converted into equivalent Y-connected sources.

However, for the purposes of analysis, Delta connected source are converted into equivalent Y-connected sources.

The analysis then follows the same procedure outlined earlier.

The analysis then follows the same procedure outlined earlier.

The equivalent phase voltage is related to the line voltage by equation (12)

The equivalent phase voltage is related to the line voltage by equation (12)

$$V_{an} = \frac{V_{ab}}{\sqrt{3}} e^{-j30^\circ}$$


The delta connected source is not widely used.

The delta connected source is not widely used.

Delta connected Loads

Three phase loads are connected in Δ configuration as shown in figure 8.

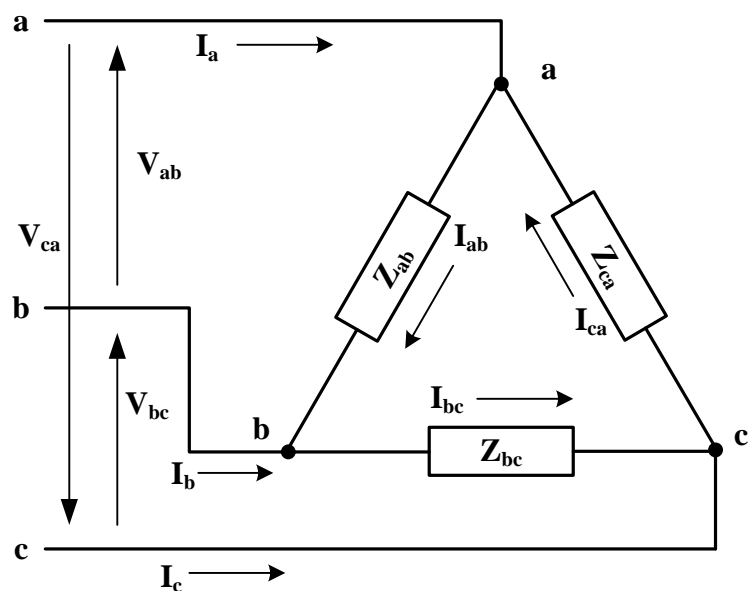Three phase loads are connected in Δ configuration as shown in figure 8.



For a balanced load, the line and phase voltages are equal.

For a balanced load, the line and phase voltages are equal.

The relationship of the phase and line currents is derived as follows:

The relationship of the phase and line currents is derived as follows:

Using KCL, the current in line I_a is related to the phase currents I_{ab} and I_{ca}

Using KCL, the current in line I_a is related to the phase currents I_{ab} and I_{ca}

$$I_a = I_{ab} - I_{ca}$$

For a balanced load, the phase currents are equal but shifted by angle of 120 degrees.

For a balanced load, the phase currents are equal but shifted by angle of 120 degrees.

Using the same procedure for determining the line voltage in the case of the Y connection,

Using the same procedure for determining the line voltage in the case of the Y connection,

$$I_a = \sqrt{3} * I_{ab} \angle -30^\circ A$$

The line current is related to the phase current by a factor of $\sqrt{3}$ and it lags it by an angle of 30 degrees.

The line current is related to the phase current by a factor of $\sqrt{3}$ and it lags it by an angle of 30 degrees.

Example 3

A 3-wire Y-connected 3-phase 120/208-V source is connected to Δ -connected balanced load. The impedance per phase is $12 \angle 30^\circ \Omega$. Find

- (i) the phase and line voltages at the load
- (ii) the phase and line currents through the load.

Solution

For a Δ connected load, the phase and line voltages are equal.

For a Δ connected load, the phase and line voltages are equal.

The voltage between the two lines(or phases) is $208 \angle 0^\circ V$.

The voltage between the two lines(or phases) is $208 \angle 0^\circ V$.

(i) $V_{ab} = V_L = 208-V$.

(ii) The phase current $I_{ab} = \frac{V_{ab}}{Z_{ab}}$

The phase current $I_{ab} = \frac{208 \angle 0^\circ}{12 \angle 30^\circ} = 17.33 \angle -30^\circ A$

The line current $I_a = \sqrt{3} * I_{ab} \angle -30^\circ A$
 $I_a = \sqrt{3} * 17.33 \angle -60^\circ A$

$$I_a = 30.0 \angle -60^\circ A$$

Summary

Summary

- In balanced "Y" circuits, line voltage is equal to phase voltage times the square root of 3, while line current is equal to phase current.

In balanced "Y" circuits, line voltage is equal to phase voltage times the square root of 3, while line current is equal to phase current.

$$V_{ab} = V_a * \sqrt{3} \angle 30^\circ$$

$$I_l = I_p$$

- In balanced Δ circuits, line voltage is equal to phase voltage, while line current is equal to phase current times the square root of 3.

In balanced Δ circuits, line voltage is equal to phase voltage, while line current is equal to phase current times the square root of 3.

$$I_a = \sqrt{3} * I_{ab} \angle -30^\circ A$$

$$V_{ab} = V_a$$